

# MCC125 Wireless link project

## Mid-term presentation

Microwave Surfers Group

Bingcheng Chen

Filip Aldebrink

Geo Philip Muppathiyil

Jiquan Mao

Malik Fahd




Link budget


# Design specifications

- RF frequency: 2.4 GHz
- 64-QAM as modulation
- 10Mbit/s data rate (Later, we found that the hardware can not support it)
- Distance of 100 m
- With BER =  $1e-6$   $\rightarrow$  SNR=26.8dB

# Proposed RX block diagram

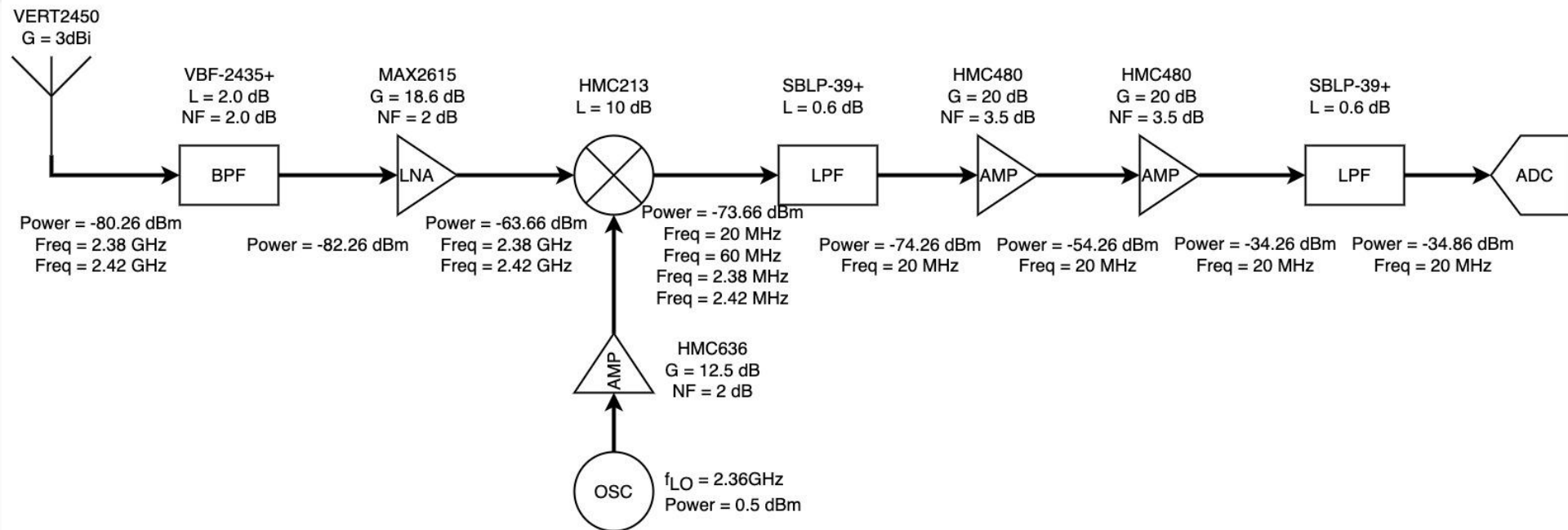

# Proposed TX block diagram

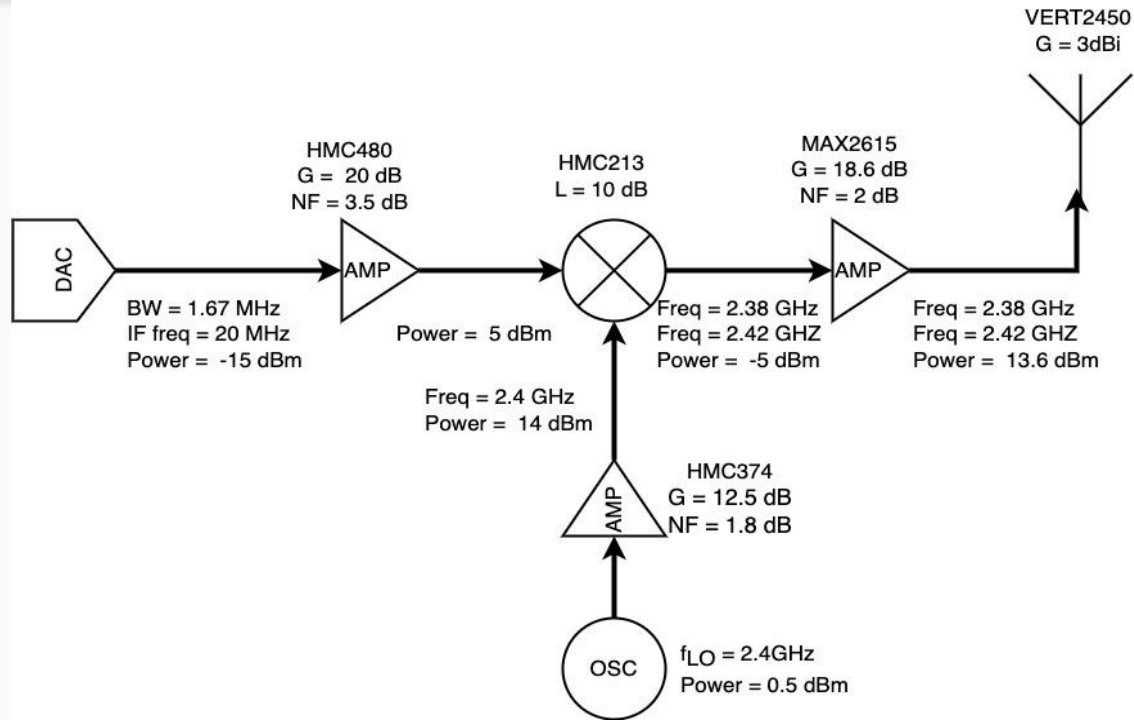



# Link budget results

- Receiver noise figure  $NF=4.74$  dB
- Transmitter linearity  $P1dB=18.3$  dBm
- Free-space loss  $FSPL=-80$  dB
- Noise power  $P_n=-107.4$  dB
- → Minimum transmit power  $P_t=-6.21$  dBm

Circuit design
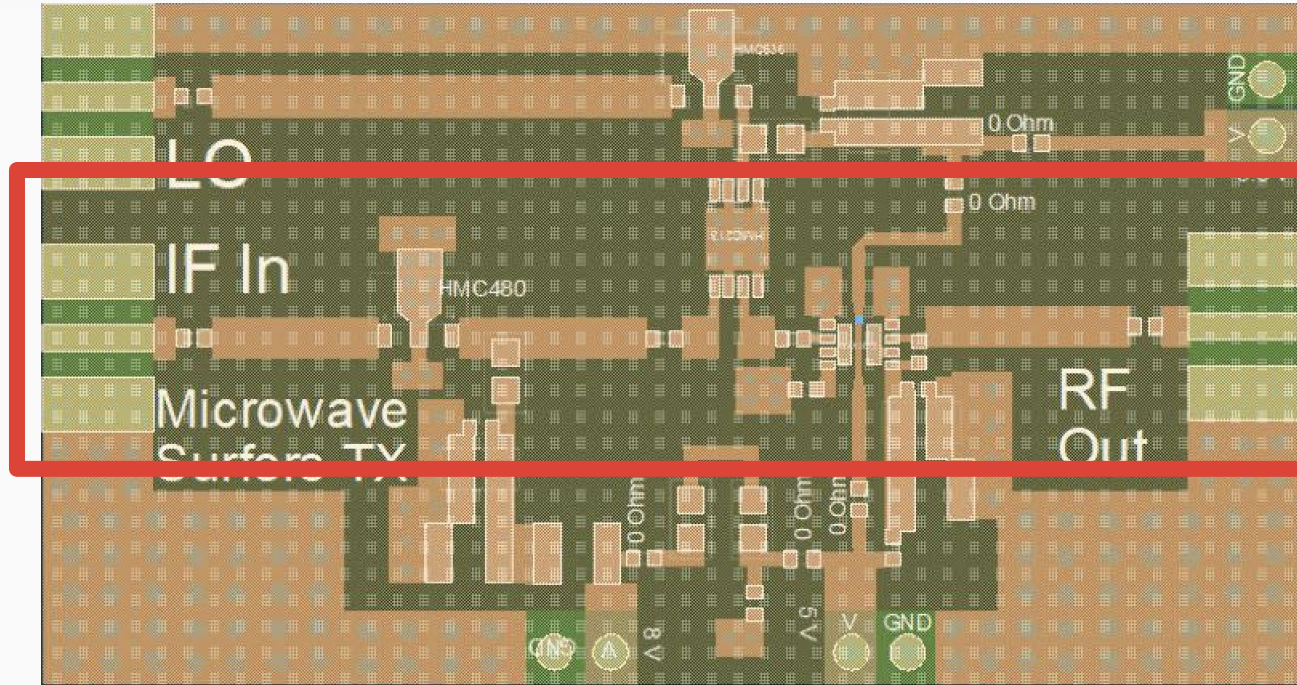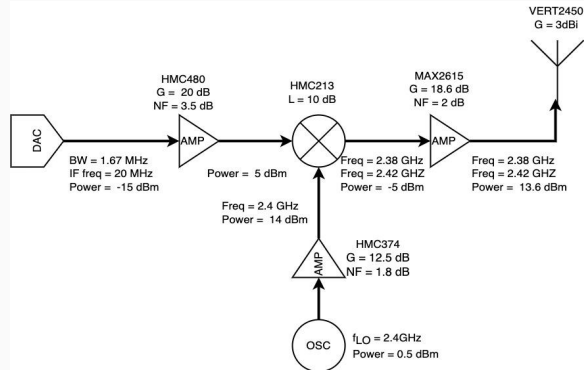
# Circuit design TX

Red rectangle represents the  
main RF line





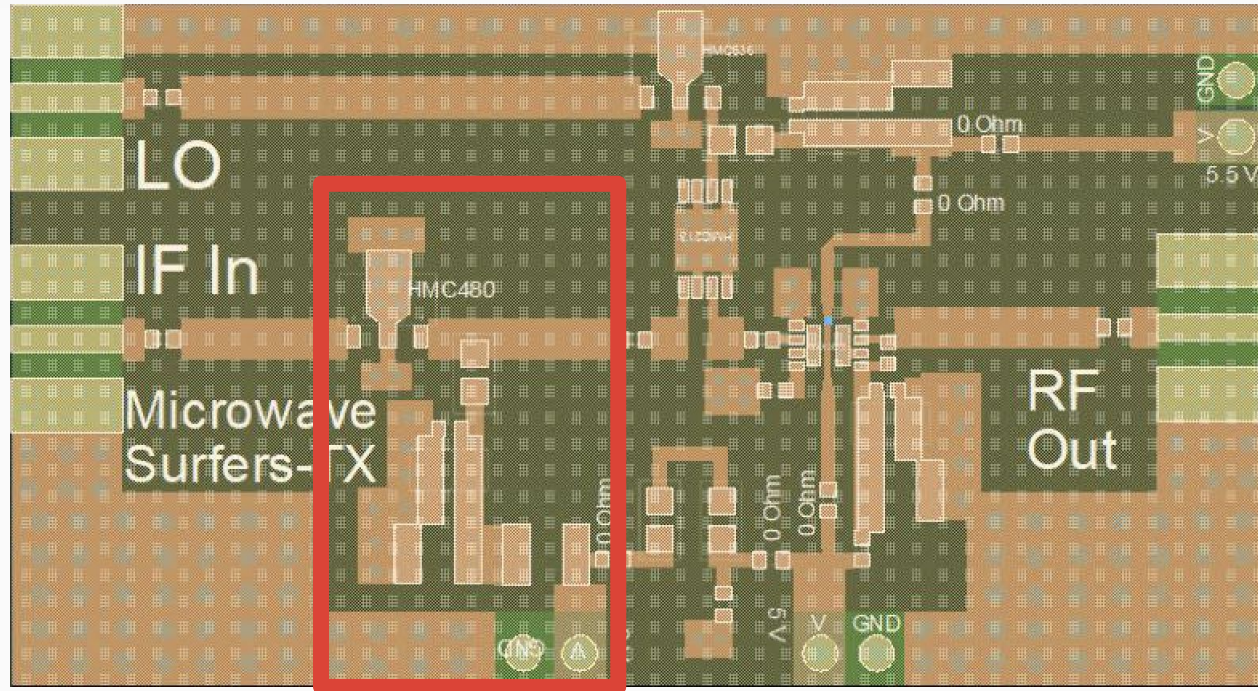
# Circuit design TX

First amplifier (HMC480) with its accompanied bias line.


The bias line consists of one series inductor, three shunted capacitors and one bias resistor. The purpose of the bias line is to insert DC into RF line and block RF in bias line.


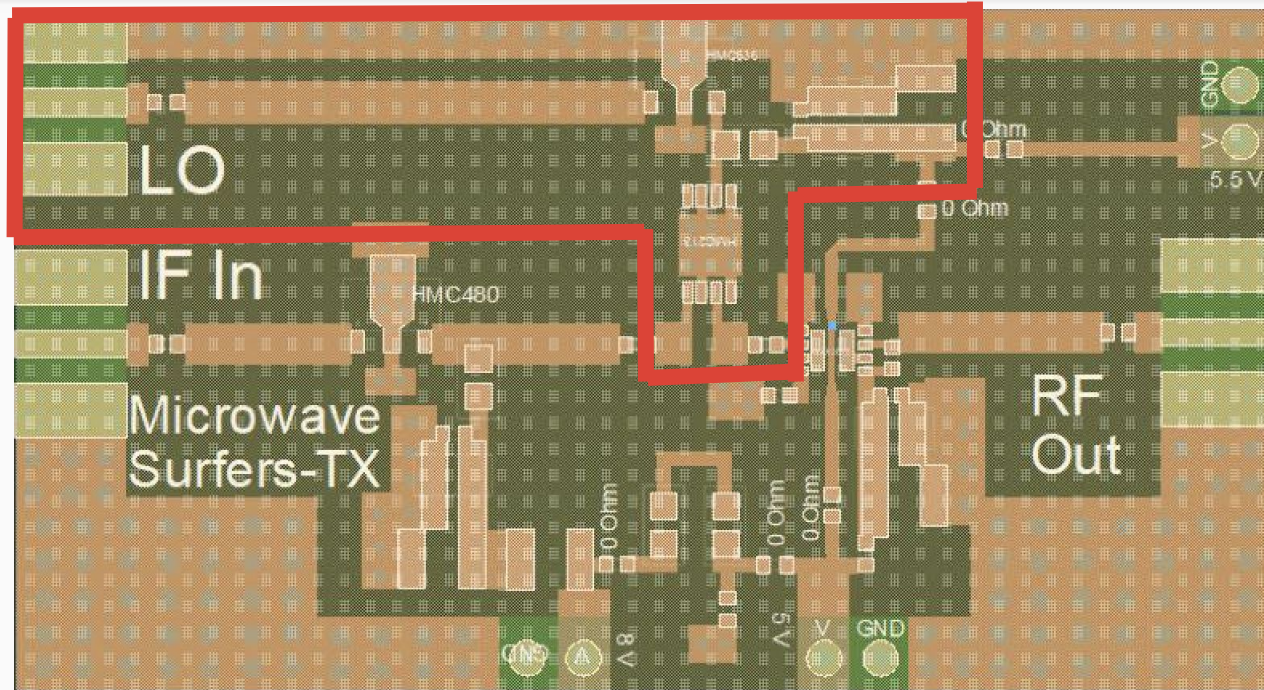
# Circuit design TX

Mixer (HMC213) fed by a  
amplifier (HMC636) which is  
fed by the LO.

The amplifier has a similar  
bias line as shown before,  
only difference is that this  
bias line does not have a bias  
resistor.





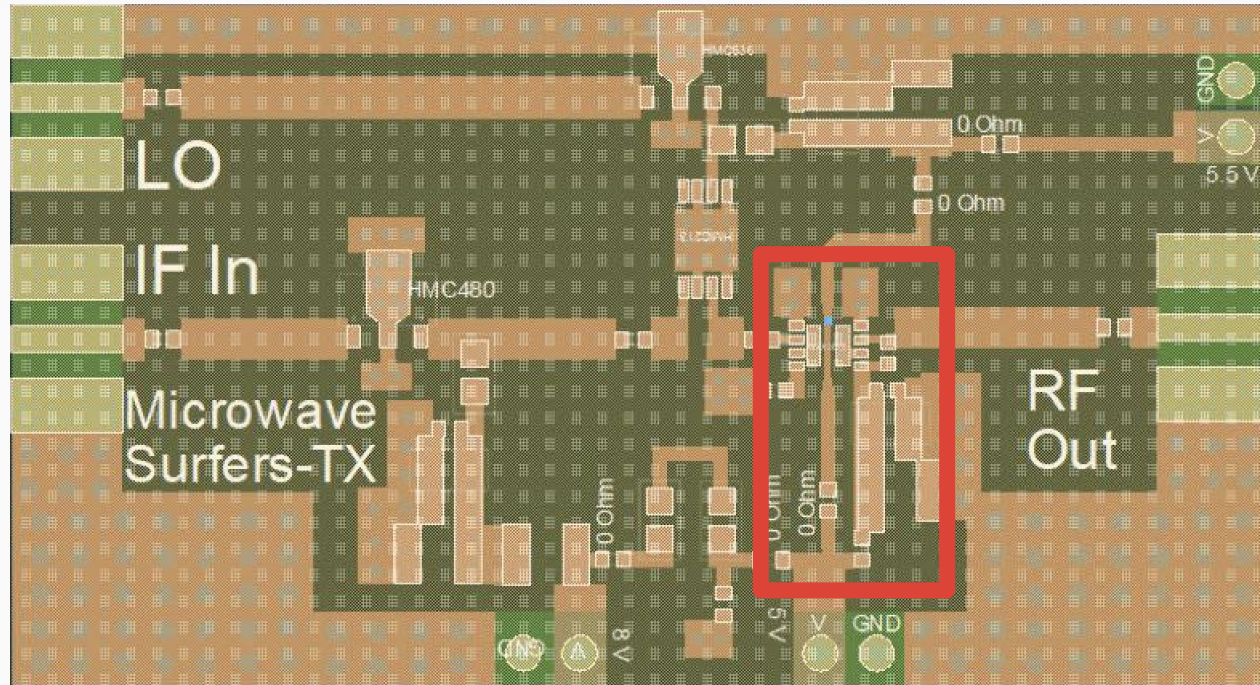
# Circuit design TX


Last amplifier (MAX2615) in  
RF line.

Has, as all the other  
amplifiers, a similar bias line.



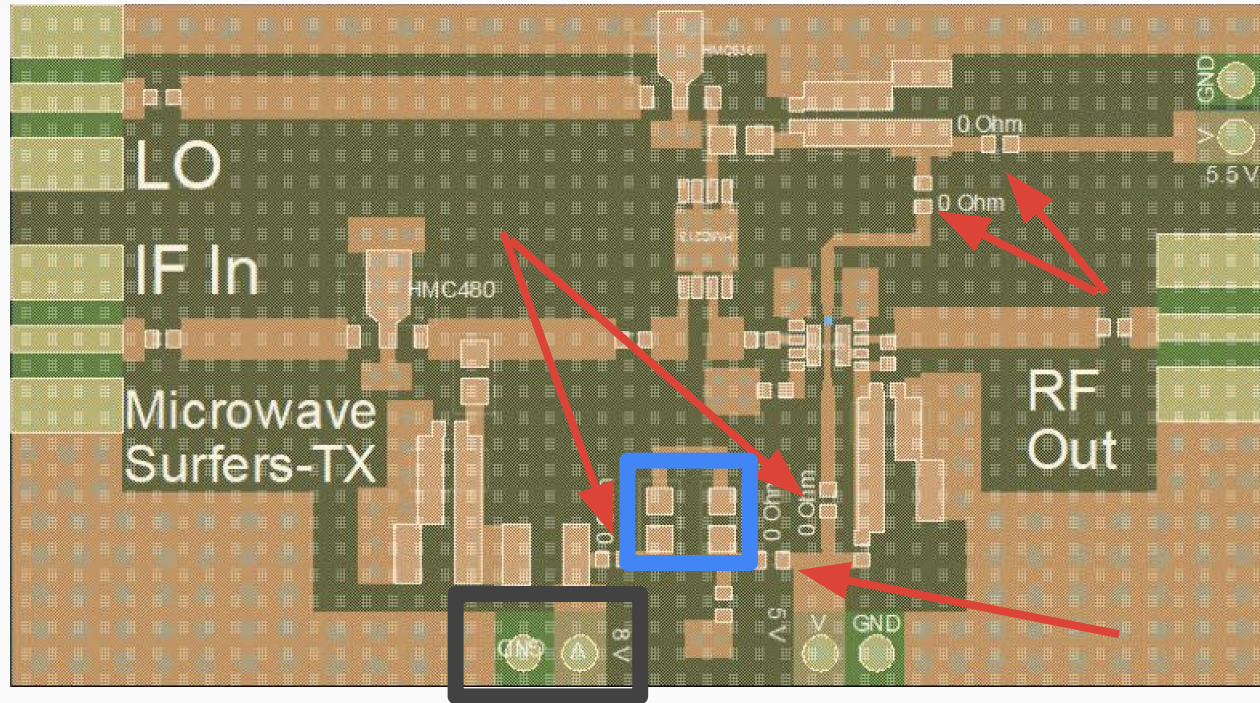
# Circuit design TX

Our vision is that we feed all bias lines with one power supply (black rectangle), by soldering the 0 Ohm resistors (red arrows) and by stepping down the voltage with 2 series resistors (blue square). If that does not work, we remove the 0 Ohm resistors and feed each bias line through its own individual power supply.






# Circuit design RX

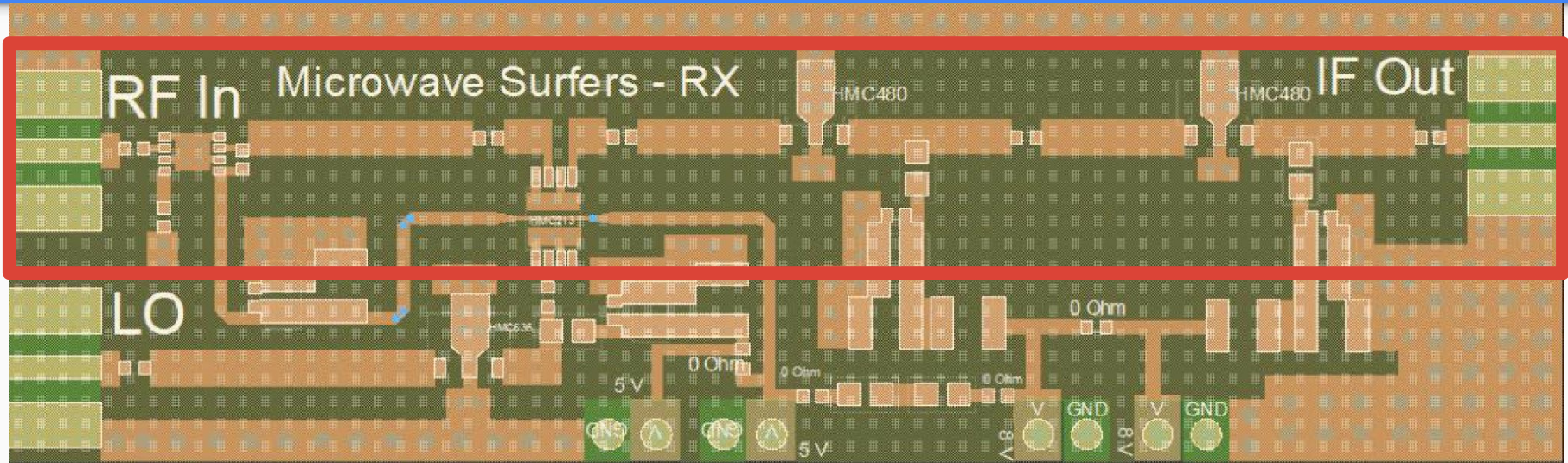

Red rectangle represents the  
main RF line


# Circuit design RX

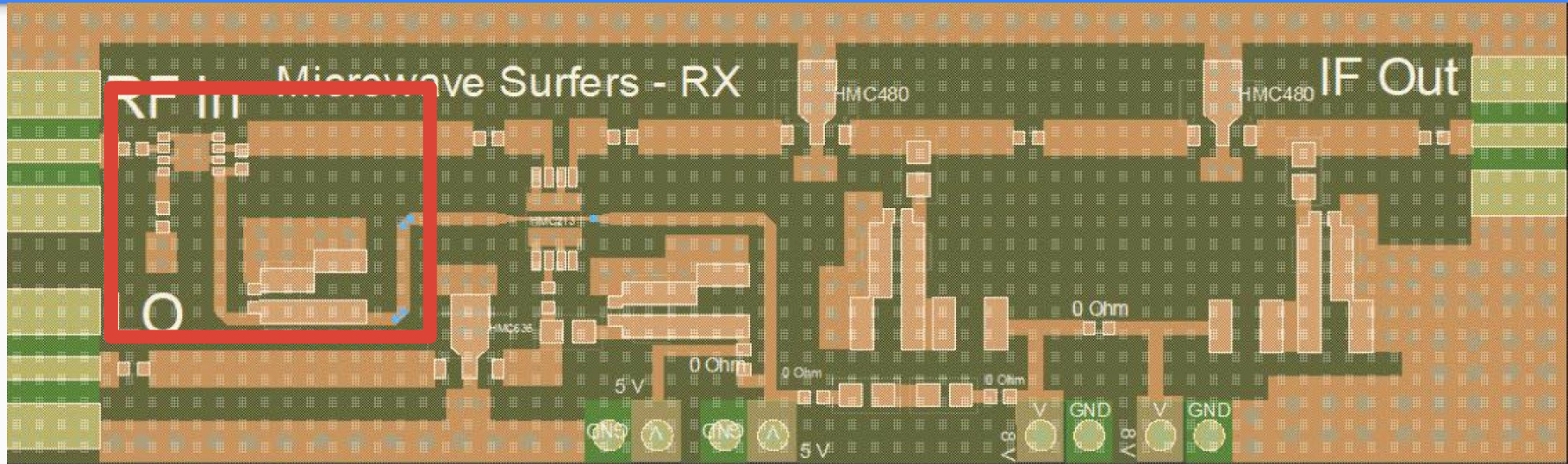

First LNA (MAX2615) with bias line (same as for the MAX2615 in the TX)




# Circuit design RX

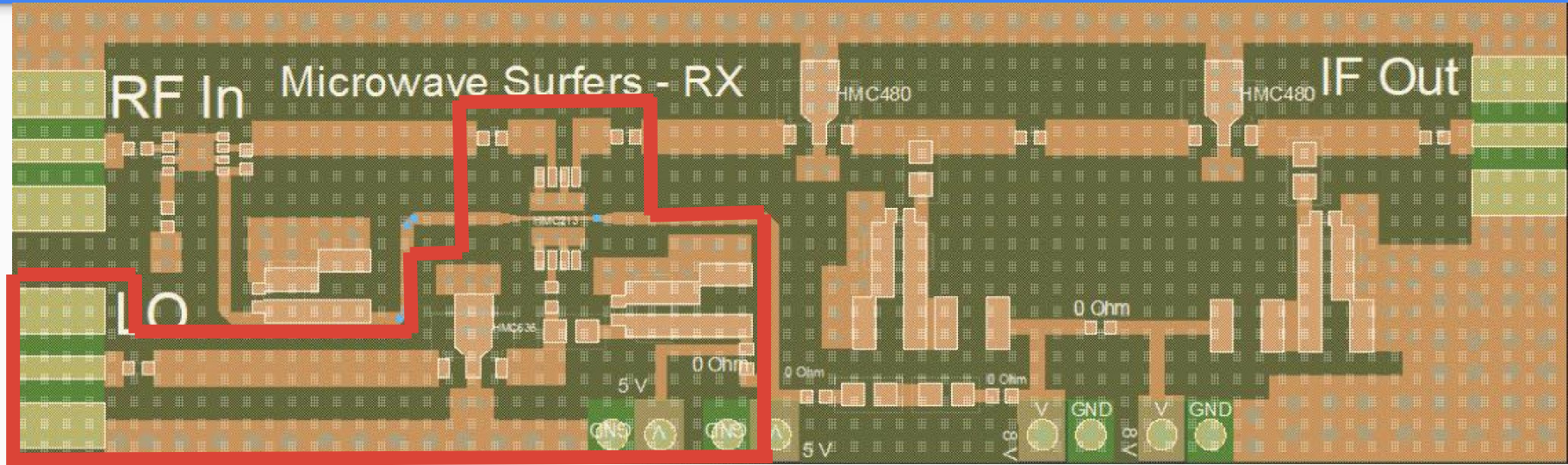

Mixer (HMC213) fed by amplifier HMC636 which is fed by LO. Amplifier has the same bias as the amplifier has in the TX.


# Circuit design RX

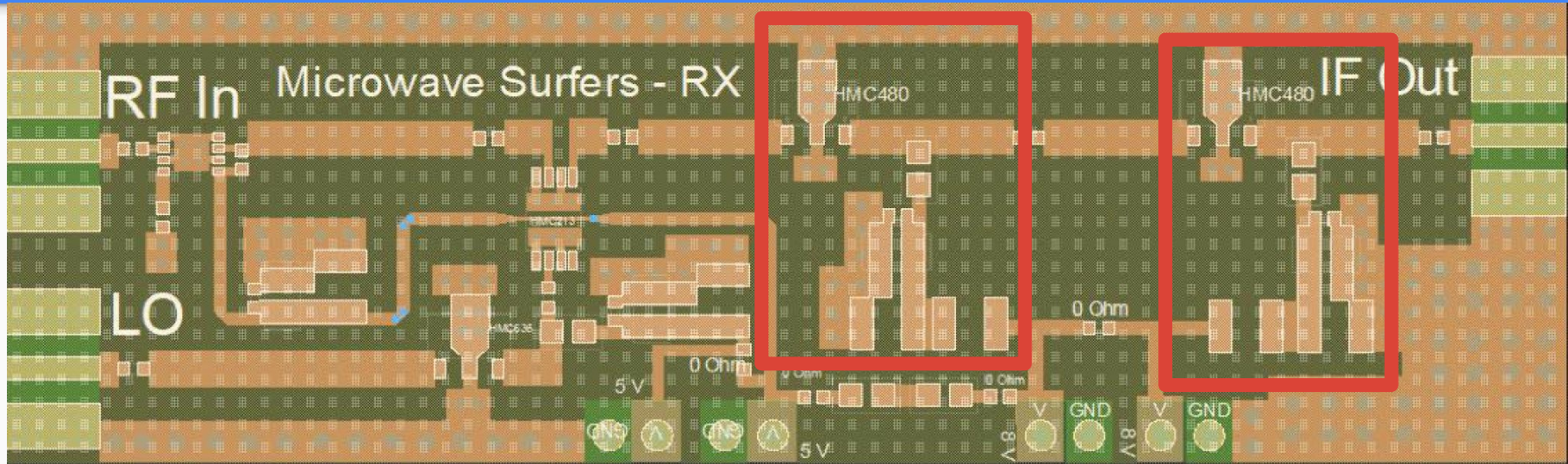

Last two (identical) amplifiers (HMC480) cascaded. Also has same bias lines as the HMC480 has in the TX.




# Circuit design RX

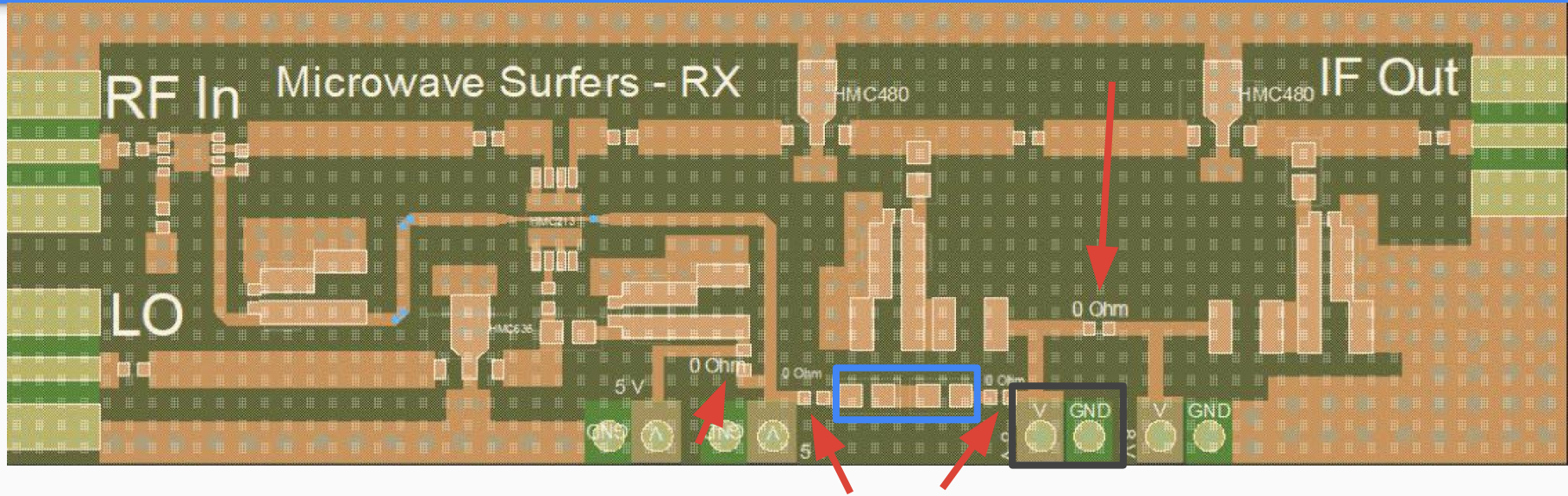


Our vision is that we feed all bias lines with one power supply (black rectangle), by soldering the 0 Ohm resistors (red arrows) and by stepping down the voltage with 2 series resistors (blue square). If that does not work, we remove the 0 Ohm resistors and feed each bias line through its own individual power supply.

# Software Design


# Transmitter Design

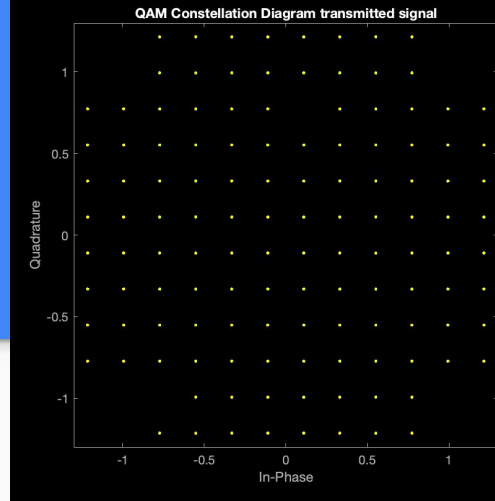

**128-QAM constellation example**

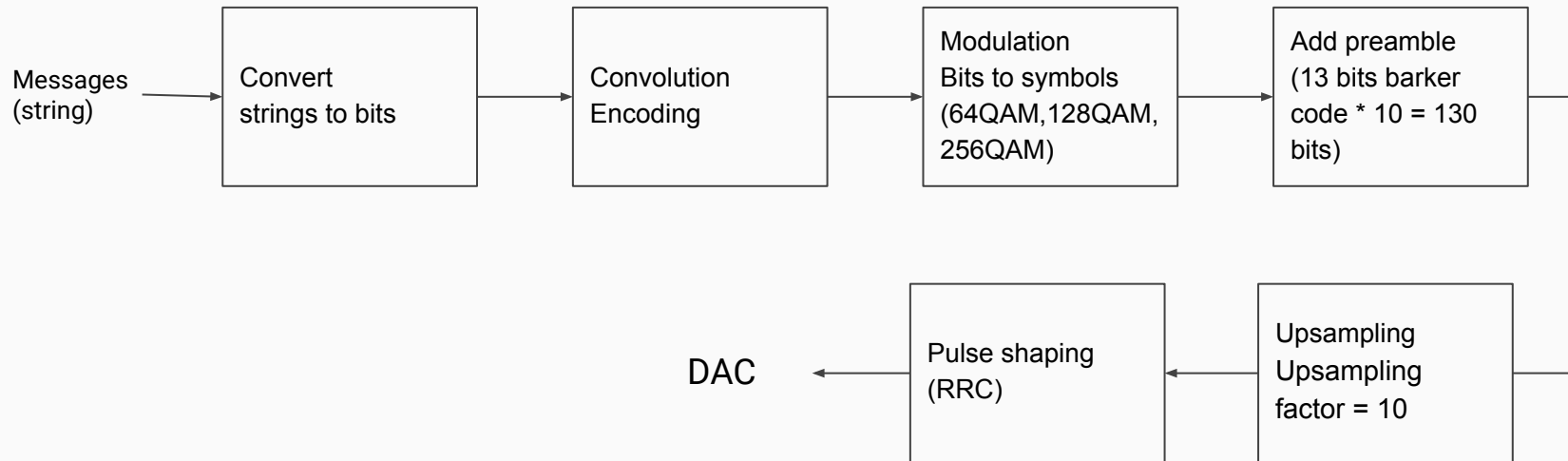

# Receiver Design

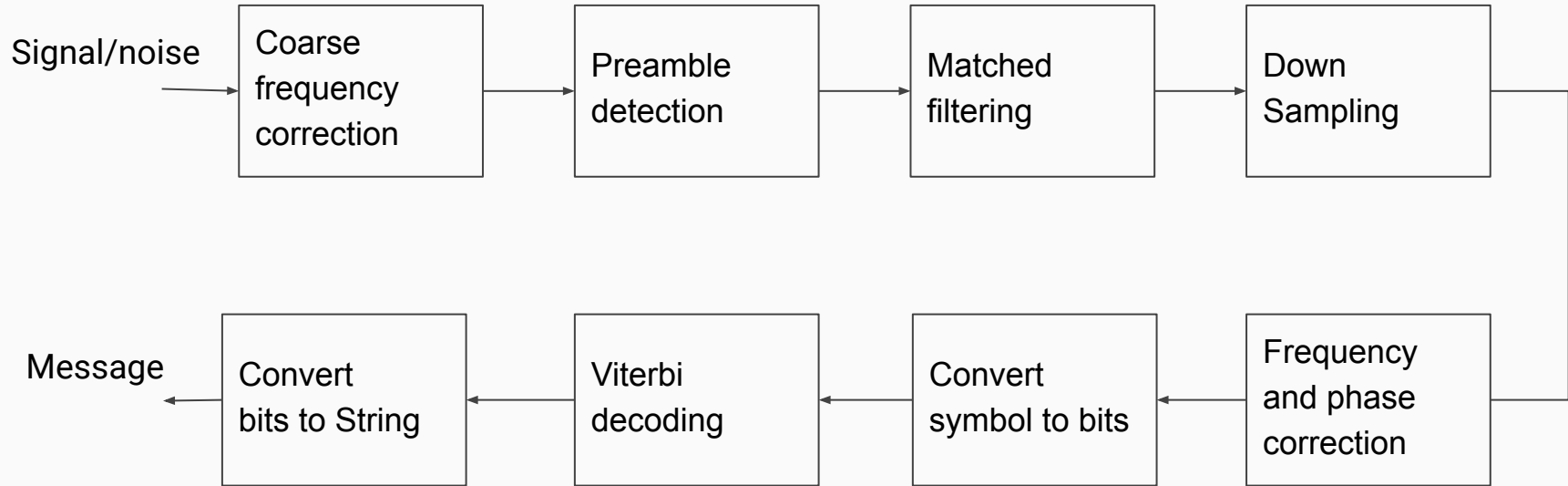

# 128-QAM (Test on the hardware provided / cable connection)

Parameters we set and got:


Interp\_factor = 70, fsfd(sample per symbol) = 10

**fs** = 100M / Interp\_factor = 1.43 MHz

Rb(bit rate) = 1 Mbits/s

**BW** = 100M / fsfd\*Interp\_factor = 143 KHz


Preamble detection

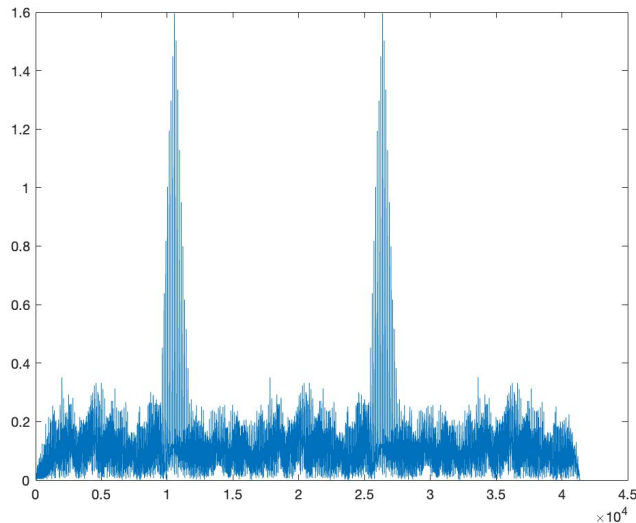

**Note: Be careful of limitations of hardware**


**Ensure stable operation by avoiding clashes when the parameter exceeds or fall below a specified value.**

Received signal

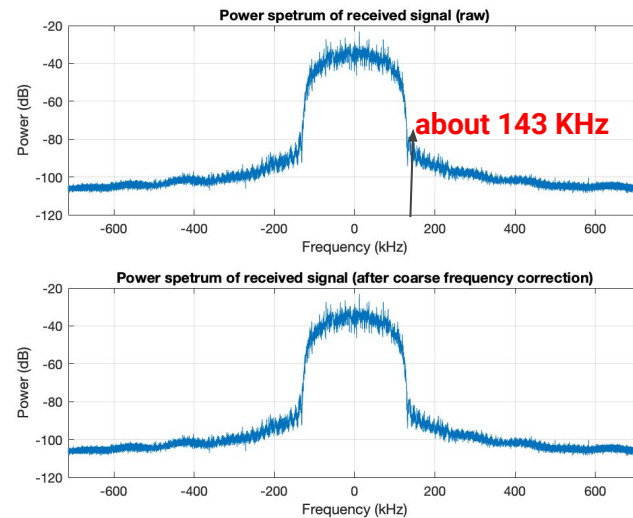


# 128-QAM (Test on the hardware provided / cable connection)


Transmitted signal

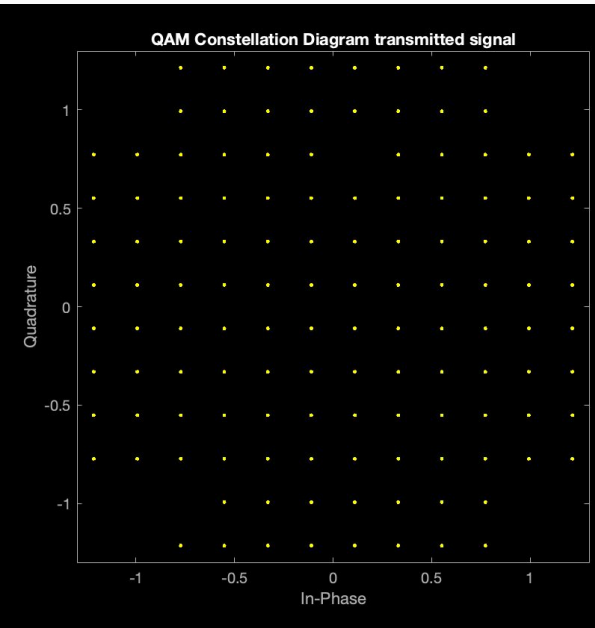

Received signal after  
downsampling

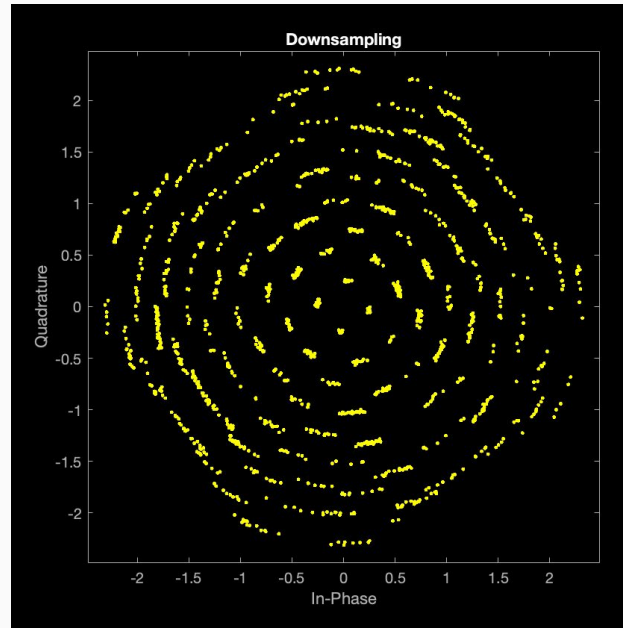

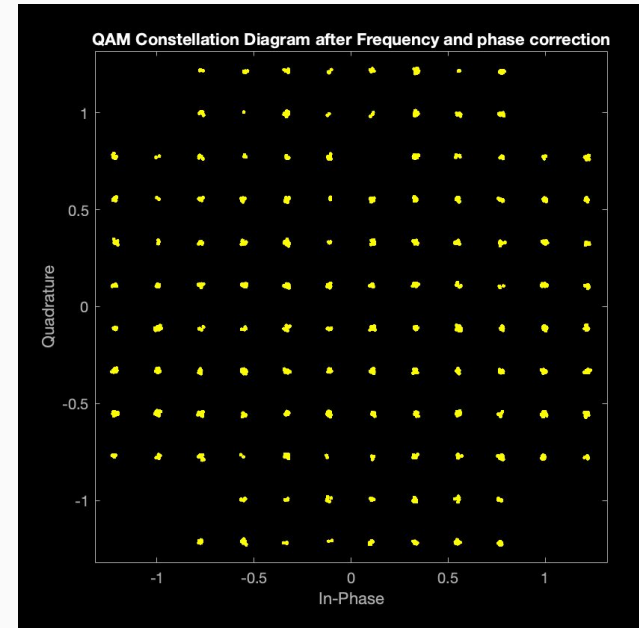Received signal after frequency  
and phase correction



Bit error (0 / 50000 bits)

# 256-QAM (Test on the hardware provided / cable connection)

Parameters we set and got:


Interp\_factor = 80, fsfd(sample per symbol) = 10

fs = 100M / Interp\_factor = 1.25 MHz


Rb(bit rate) = 1 Mbits/s

BW = 100M / fsfd\*Interp\_factor = 125 KHz

## Preamble detection

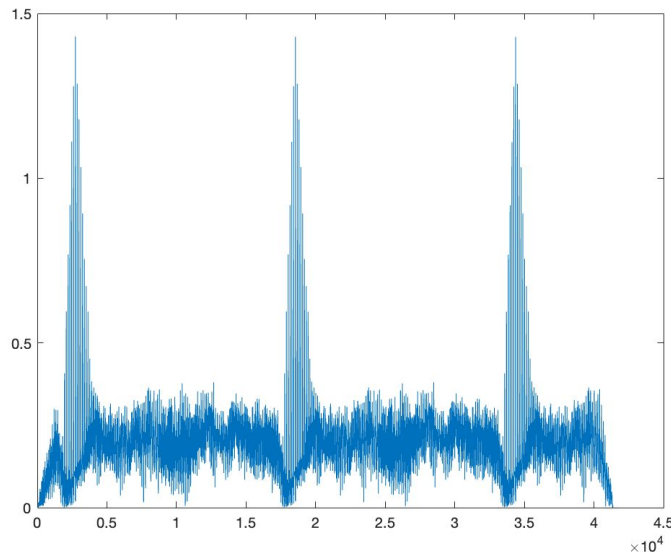


## Received signal

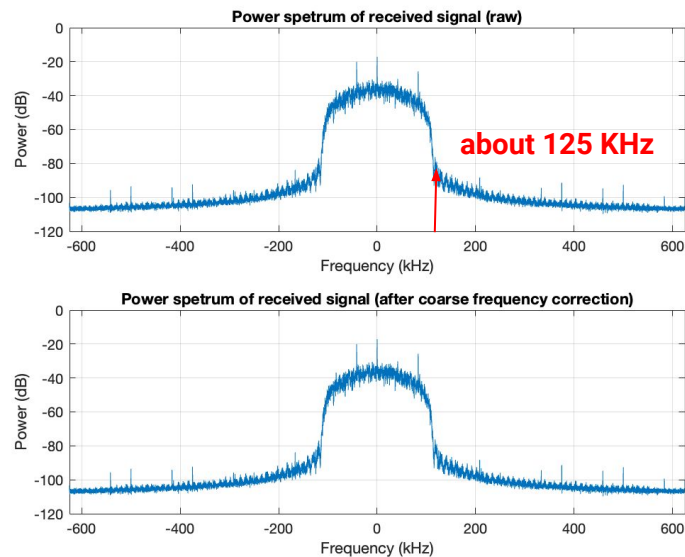


# 256-QAM (Test on the hardware provided / cable connection)


Transmitted signal

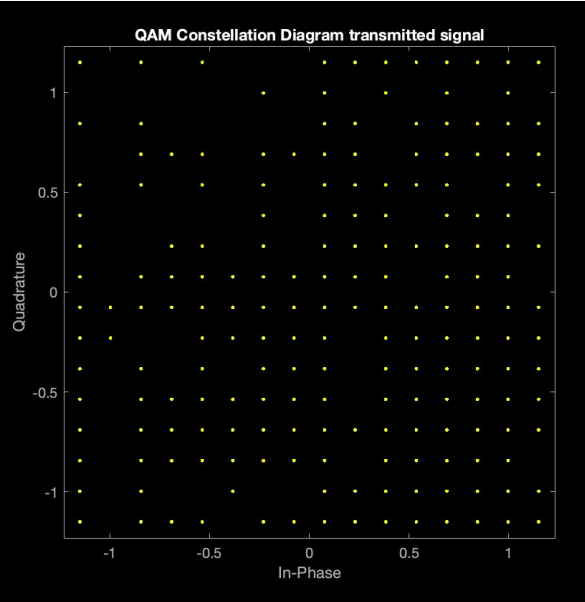

Received signal after downsampling

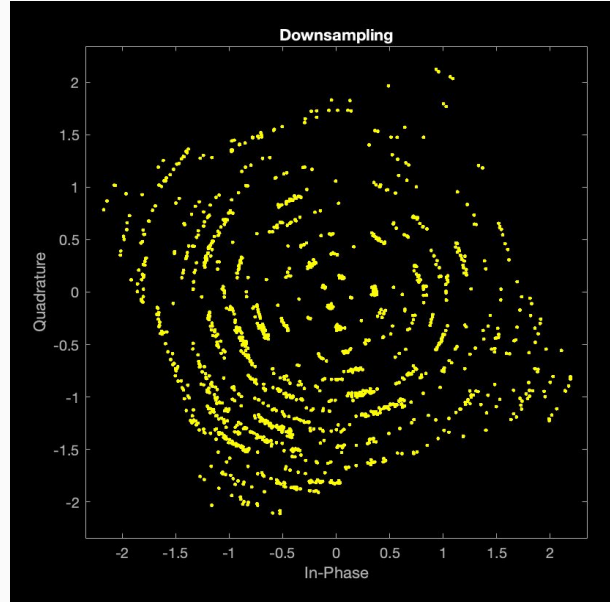

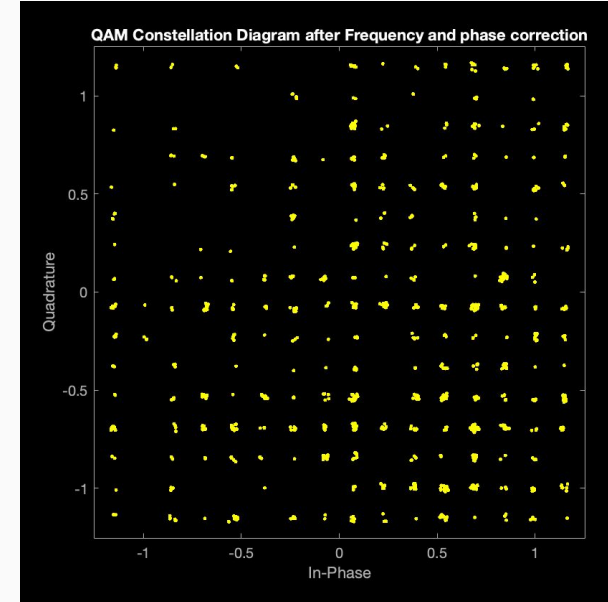Received signal after frequency and phase correction



Bit error (0/50000 bits)



# Thanks!

Contact us !

Bingcheng Chen

Filip Aldebrink

Geo Philip Muppathiyil

Jiquan Mao

Malik Fahd

